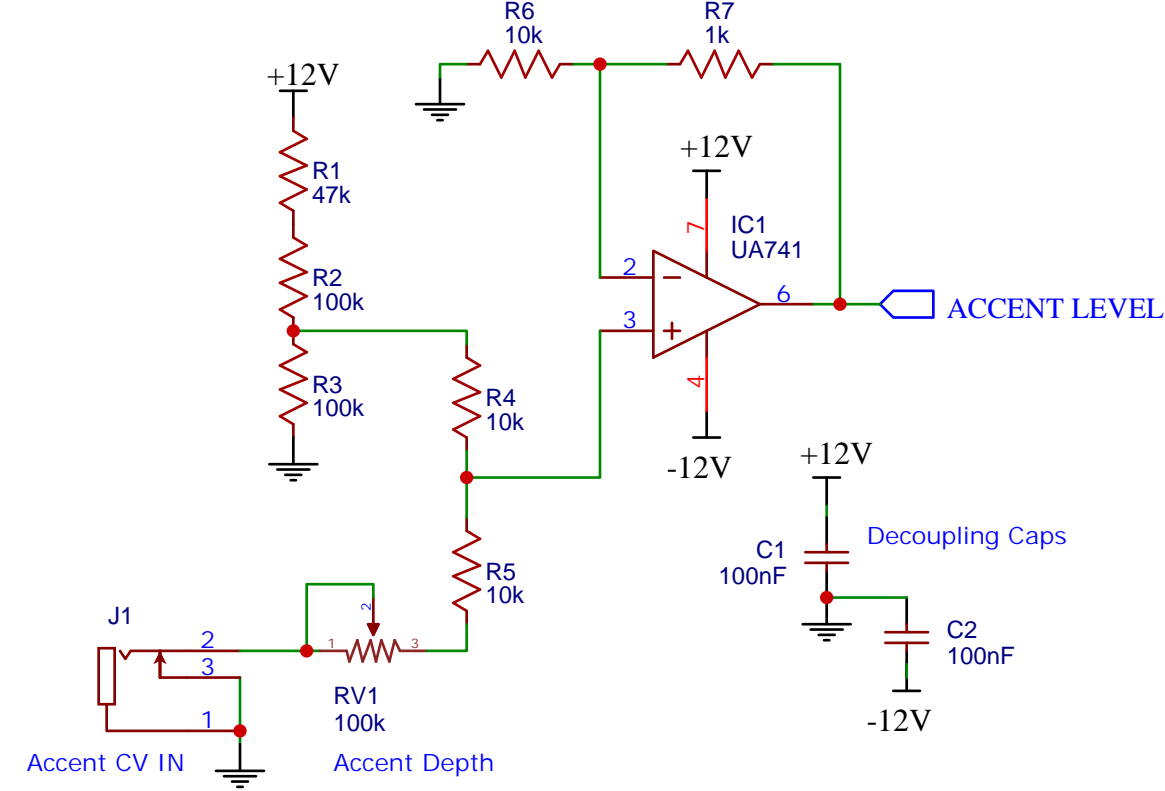




Accent Mixer

Sets the amplitude for the triggers





Trigger Logic

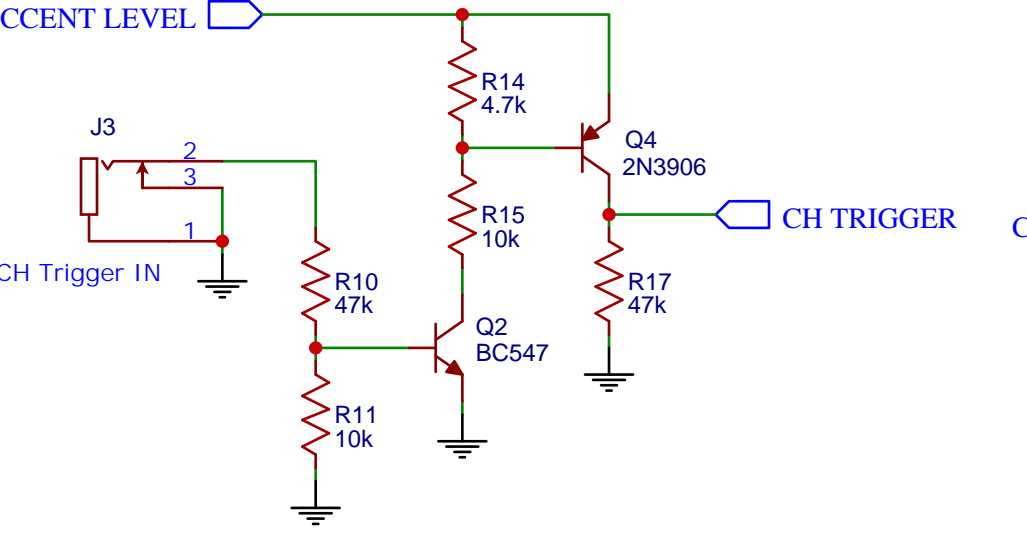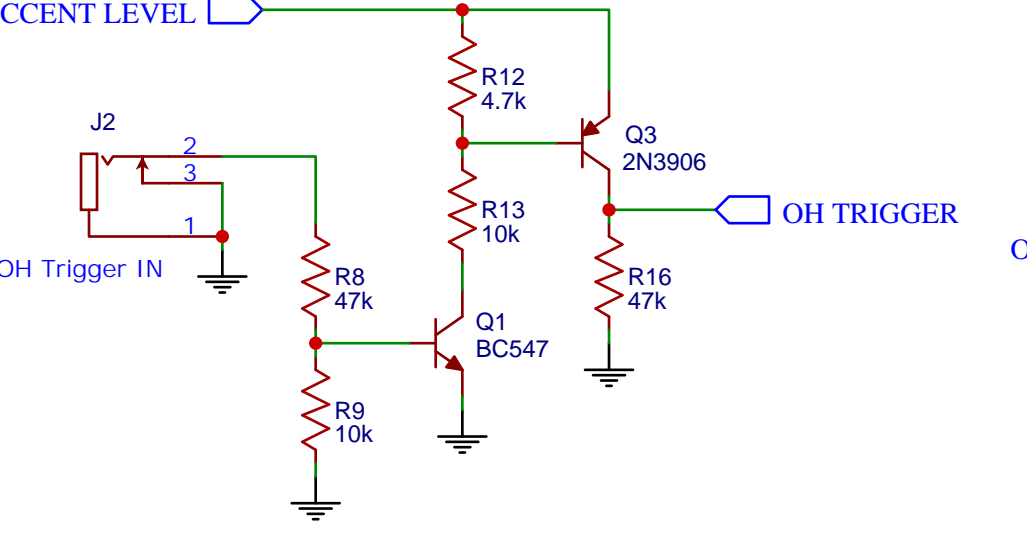Creates the internal triggers with accent levels
Based on the TR-808 service manual





Envelope Generators

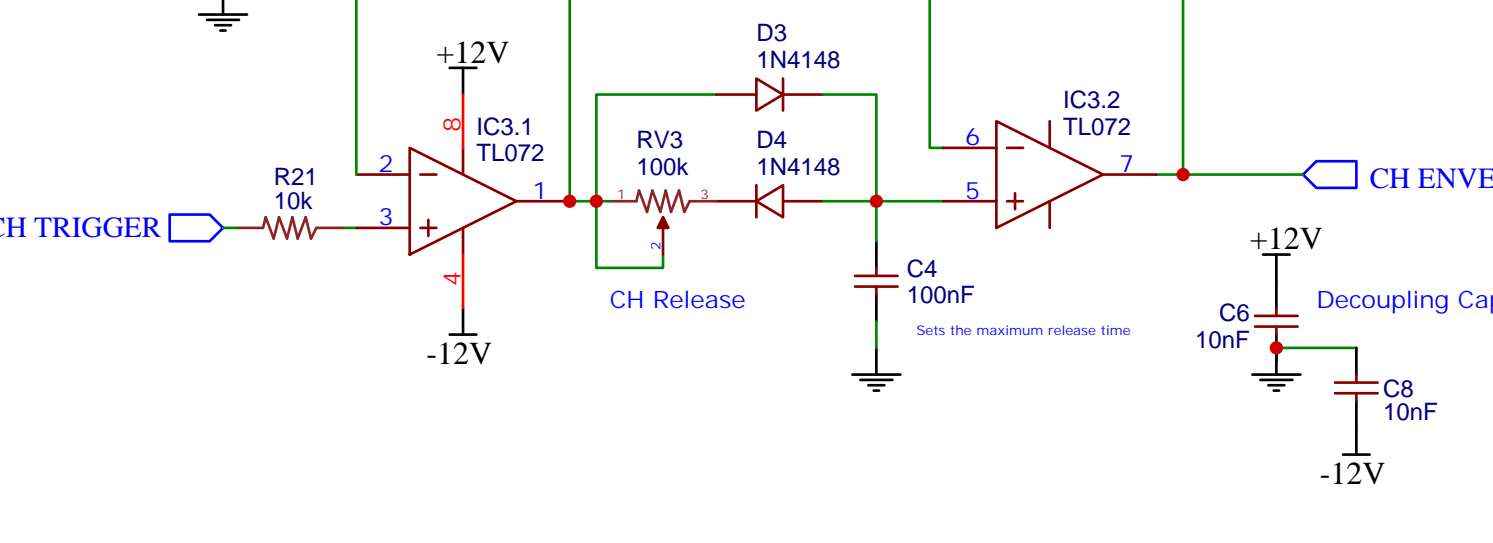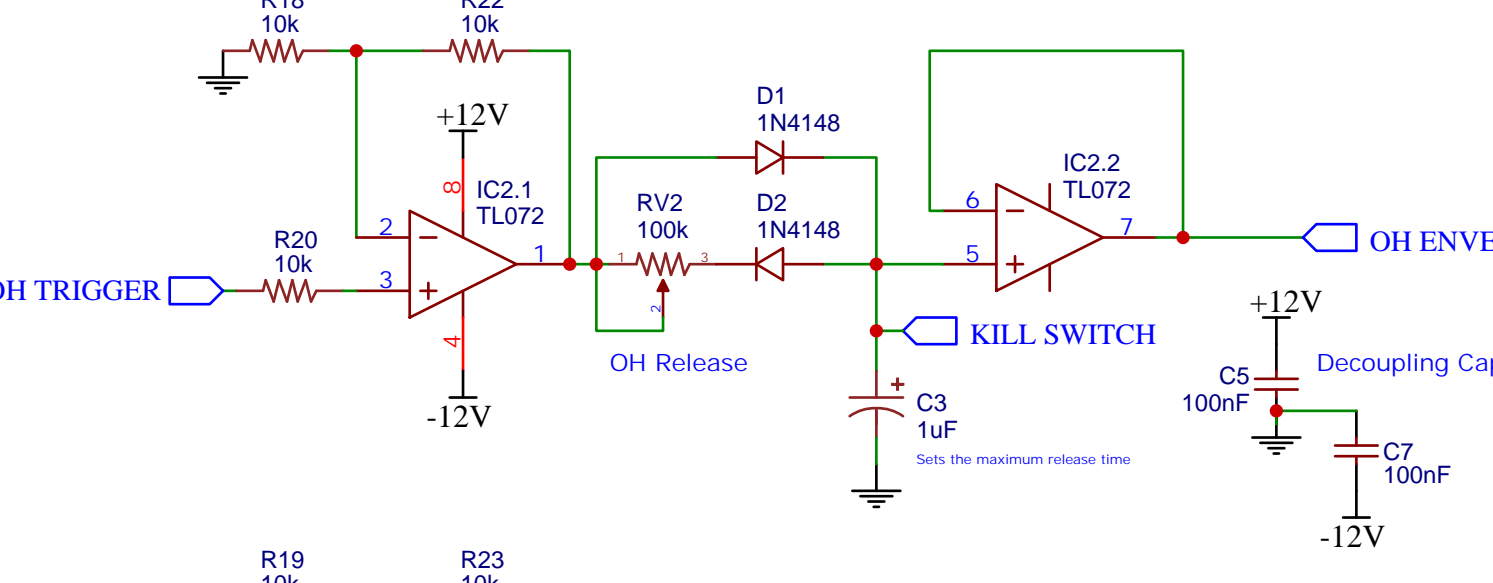Based on "simple diy envelope generator" by LOOK MUM NO COMPUTER




VCAs

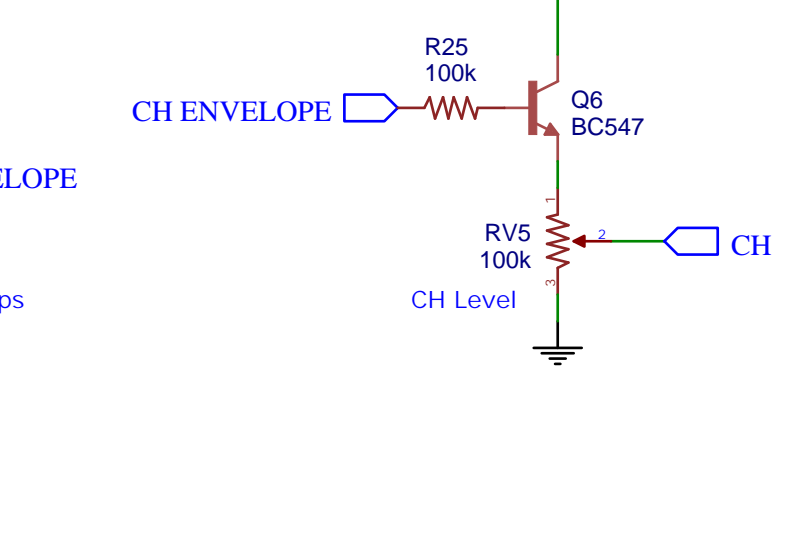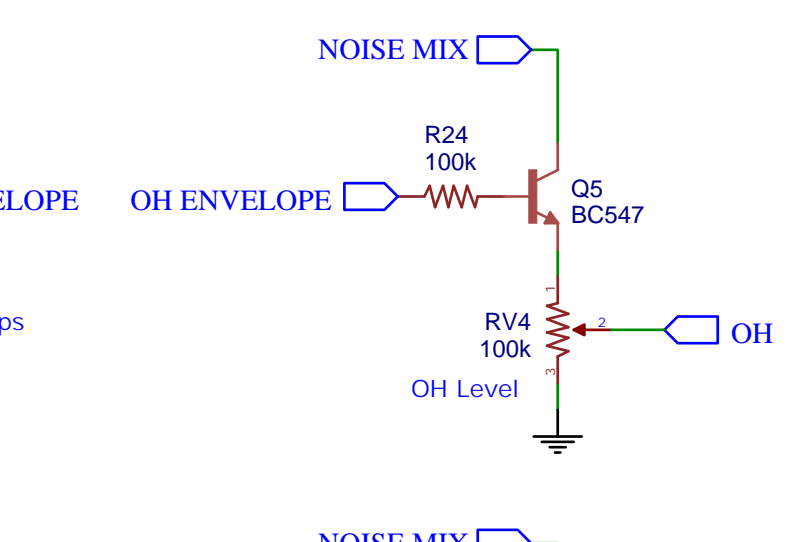Based on "LOGIC NOISE: MORE CMOS COWBELL!"
by Elliot Williams via hackaday.com





Kill Switch

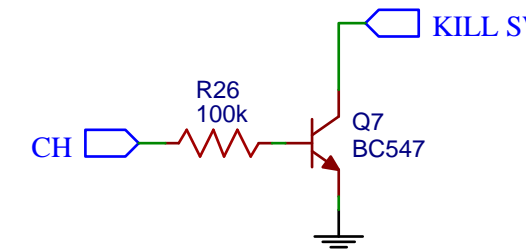CH stops the OH immediately by uncharging its release cap
Inspired by the TR-808




Amplification

Mixes the signals for the output

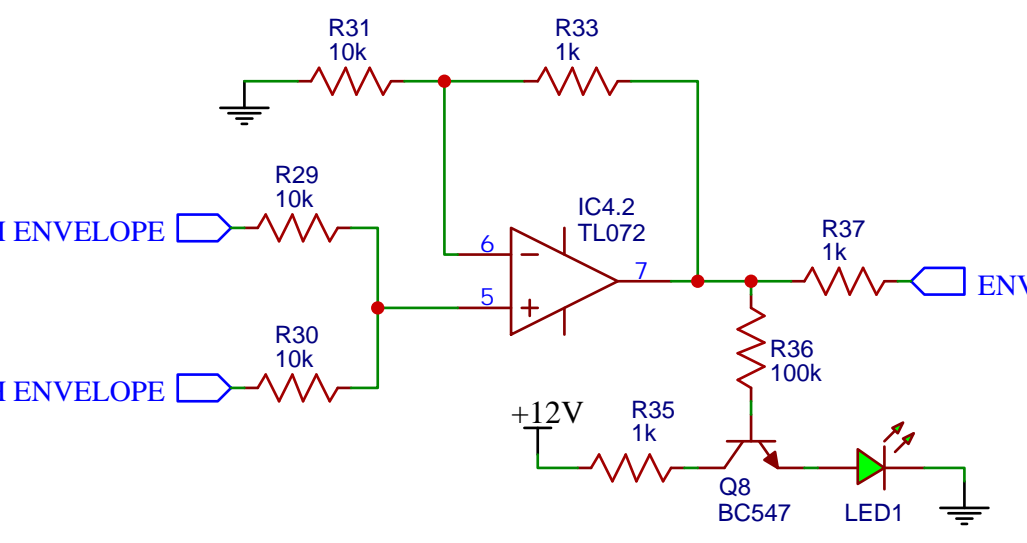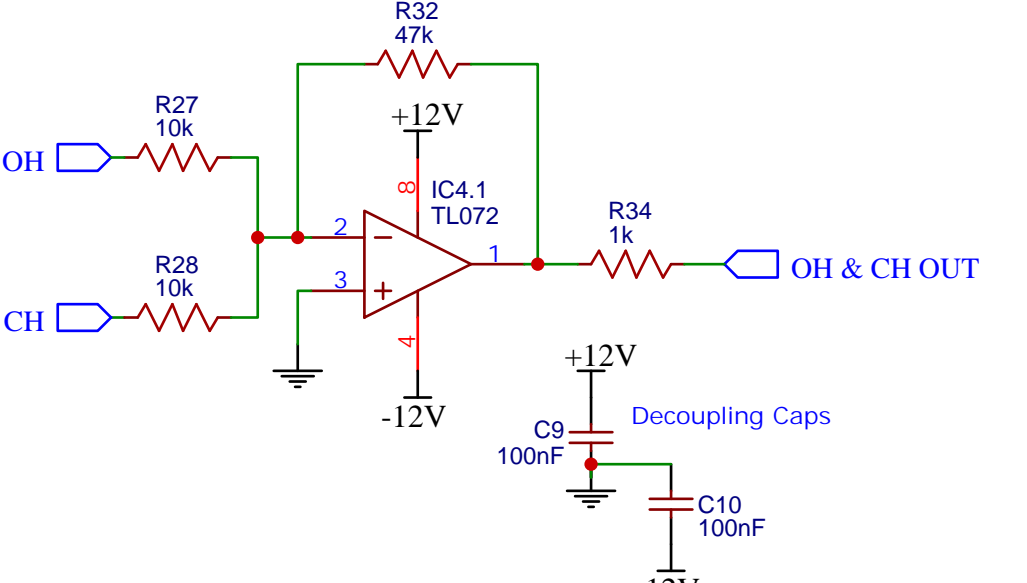


Crash (Metallic Noise)

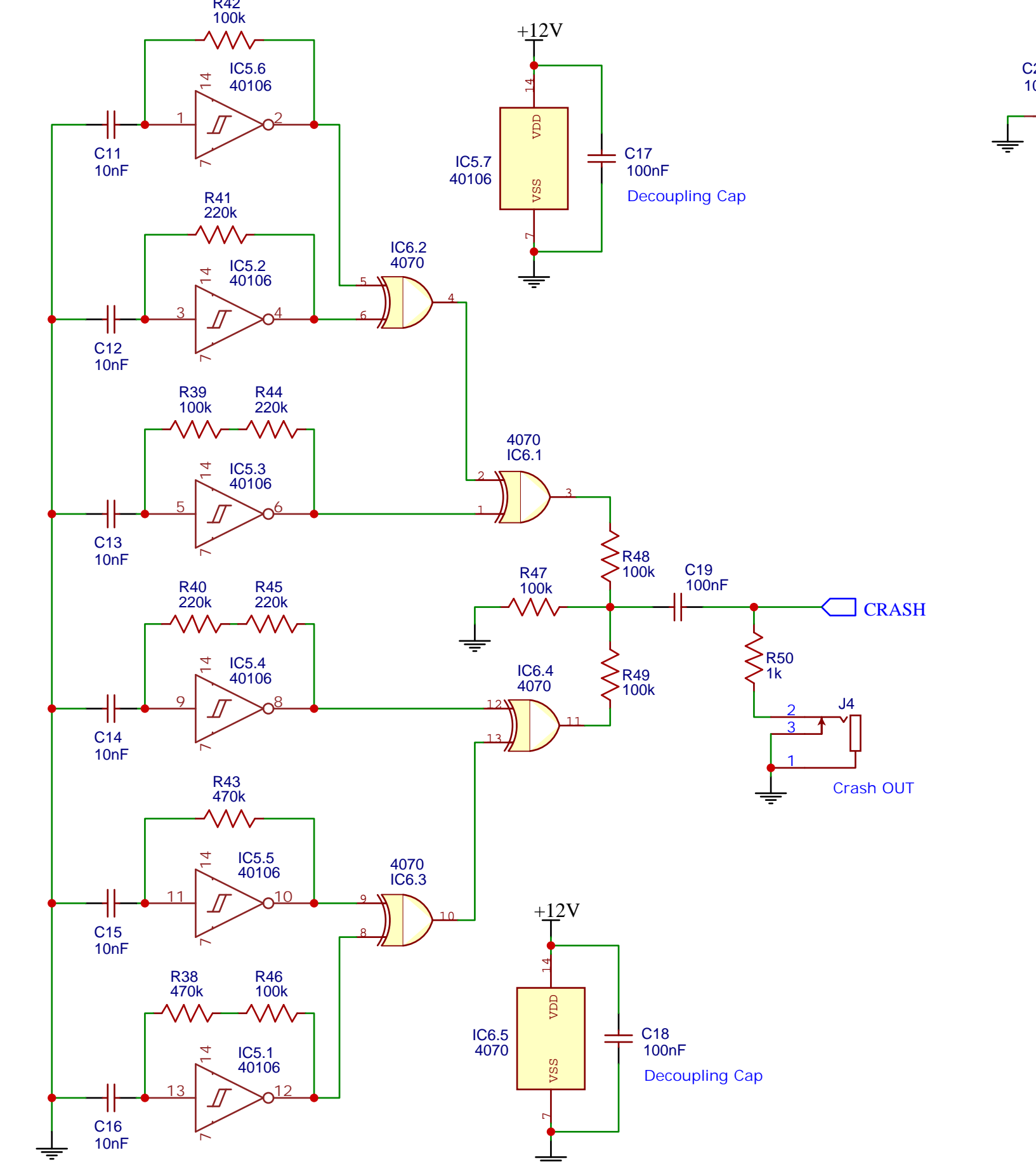Based on "LOGIC NOISE: MORE CMOS COWBELL!"
by Elliot Williams via hackaday.com



White Noise

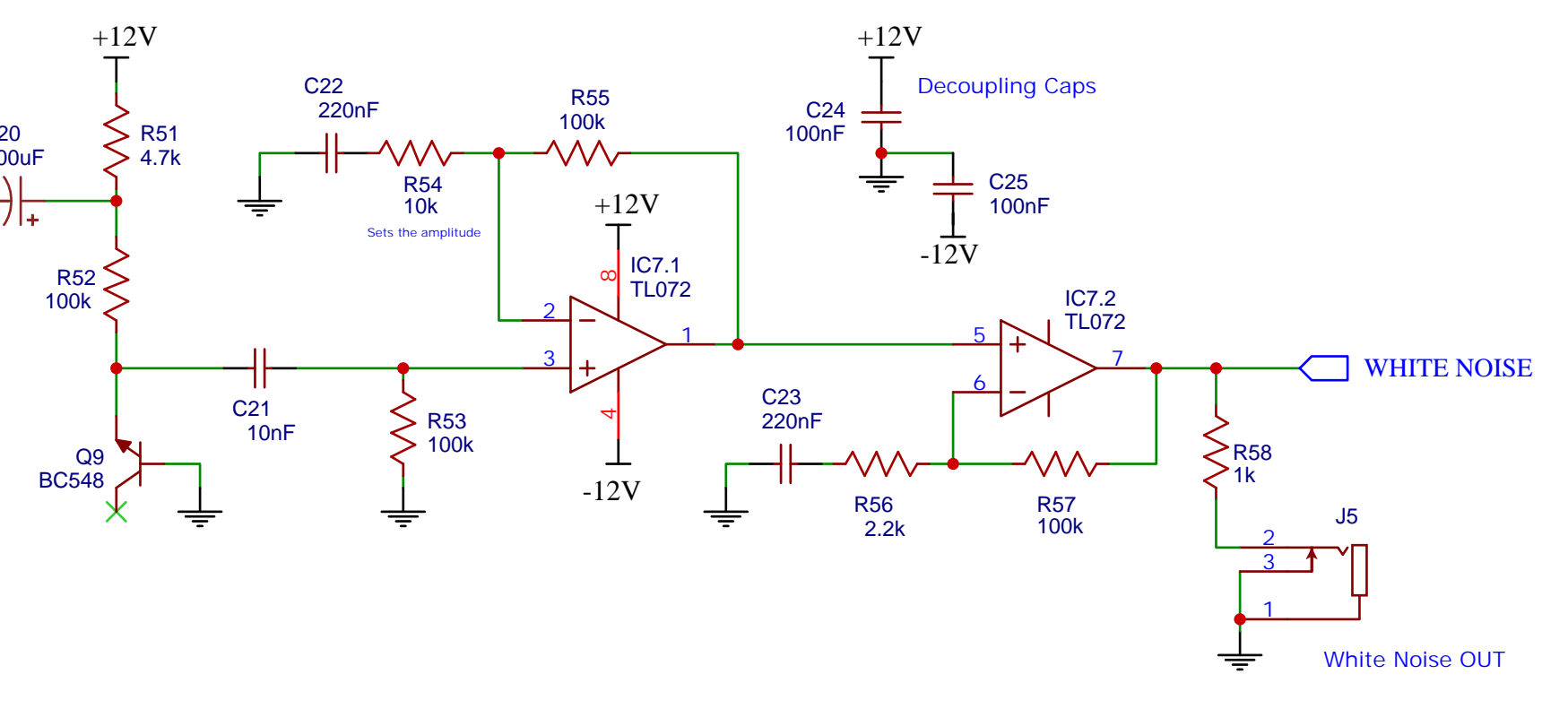Based on "White Noise Source" by René Schmitz via schmitzbits.de



Noise Mixer

Blends the two noise sources

