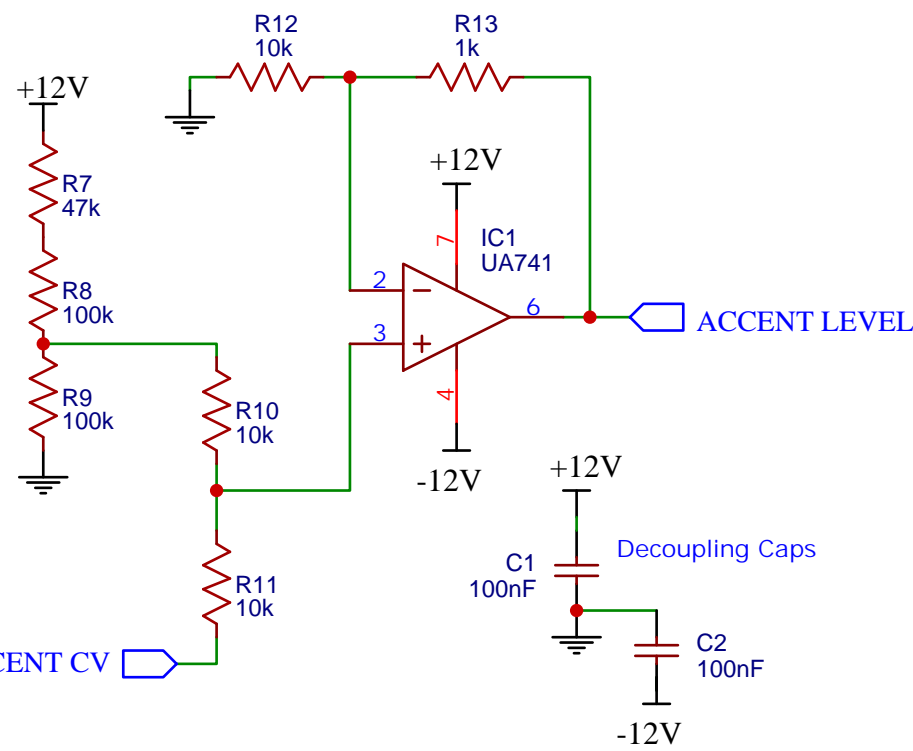


Accent Mixer


Sets the amplitude for the triggers



Trigger Logic


Creates the internal triggers with accent levels

Based on the TR-808 service manual

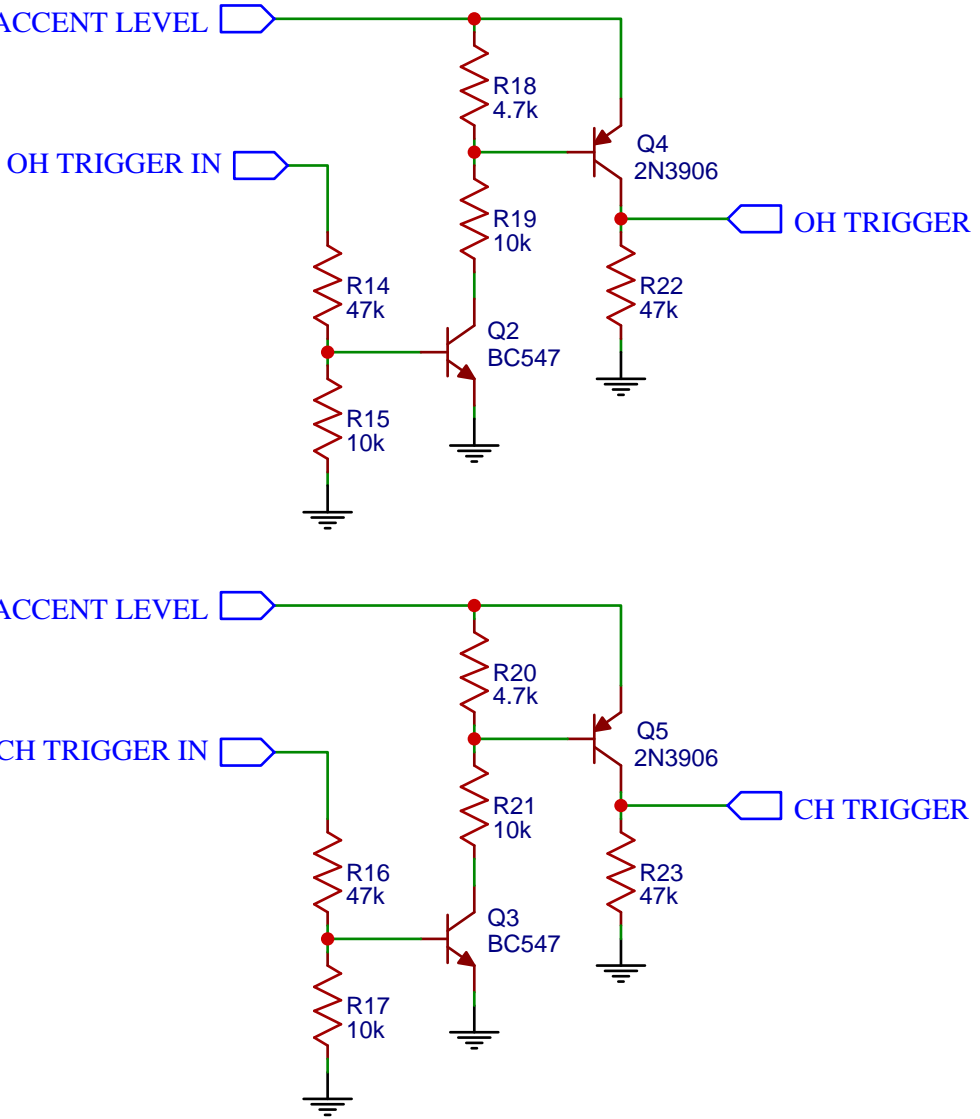


Envelope Generators

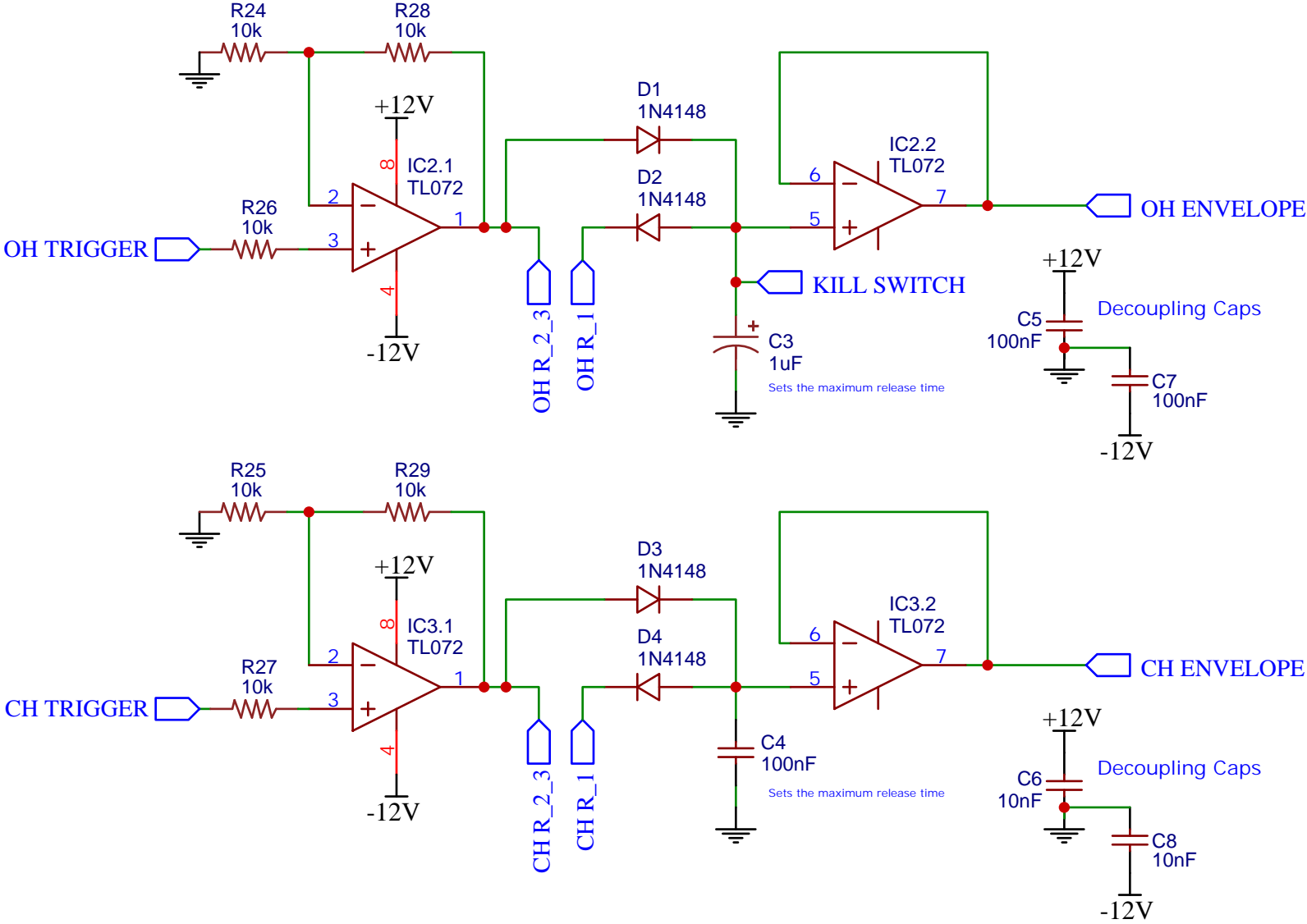Based on "simple diy envelope generator" by LOOK MUM NO COMPUTER



VCAs

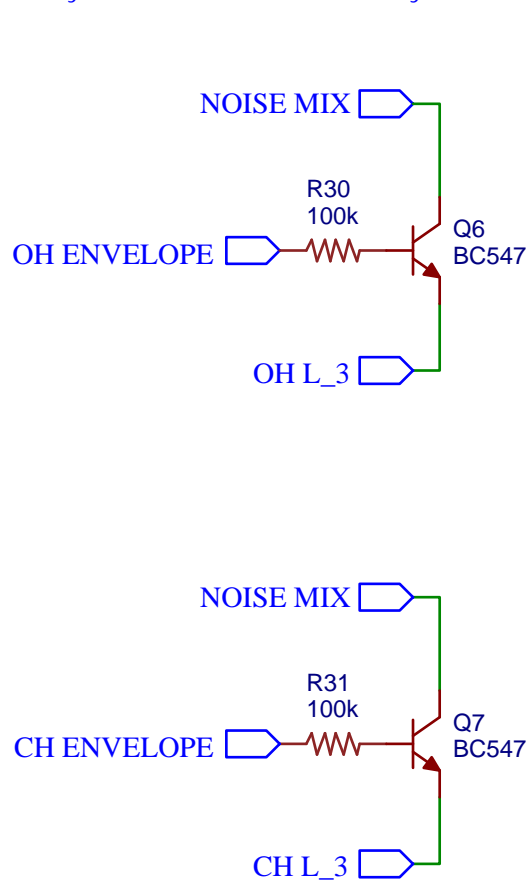
Based on "LOGIC NOISE: MORE CMOS COWBELL!" by Elliot Williams via hackaday.com



Kill Switch


CH stops the OH immediately by uncharging its release cap

Inspired by the TR-808

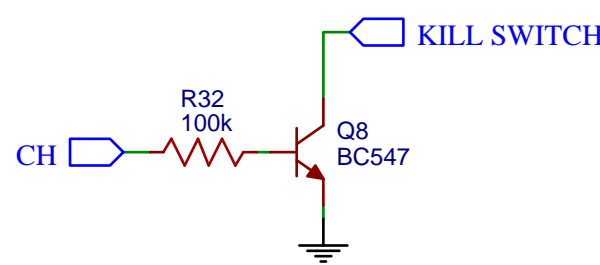


Amplification

Mixes the signals for the output

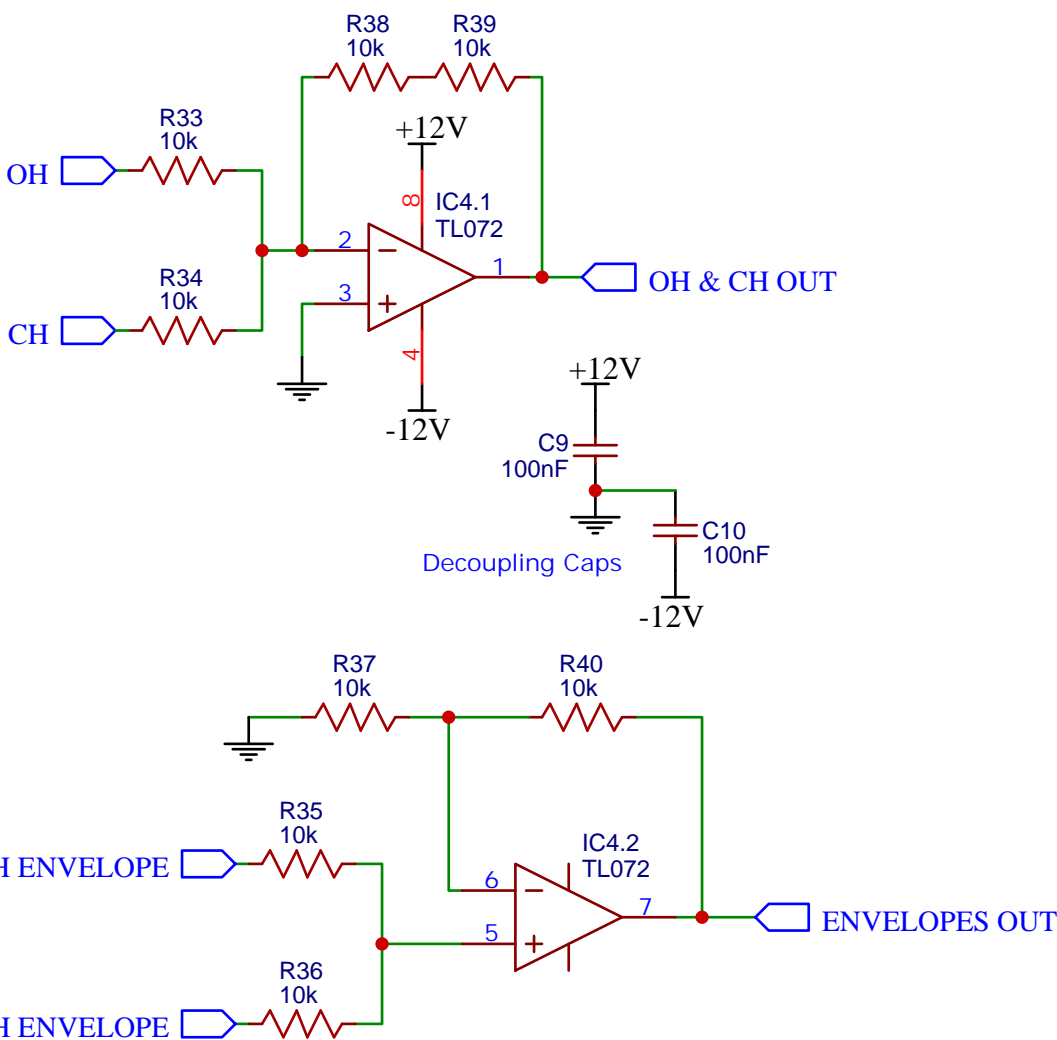


Board Connectors

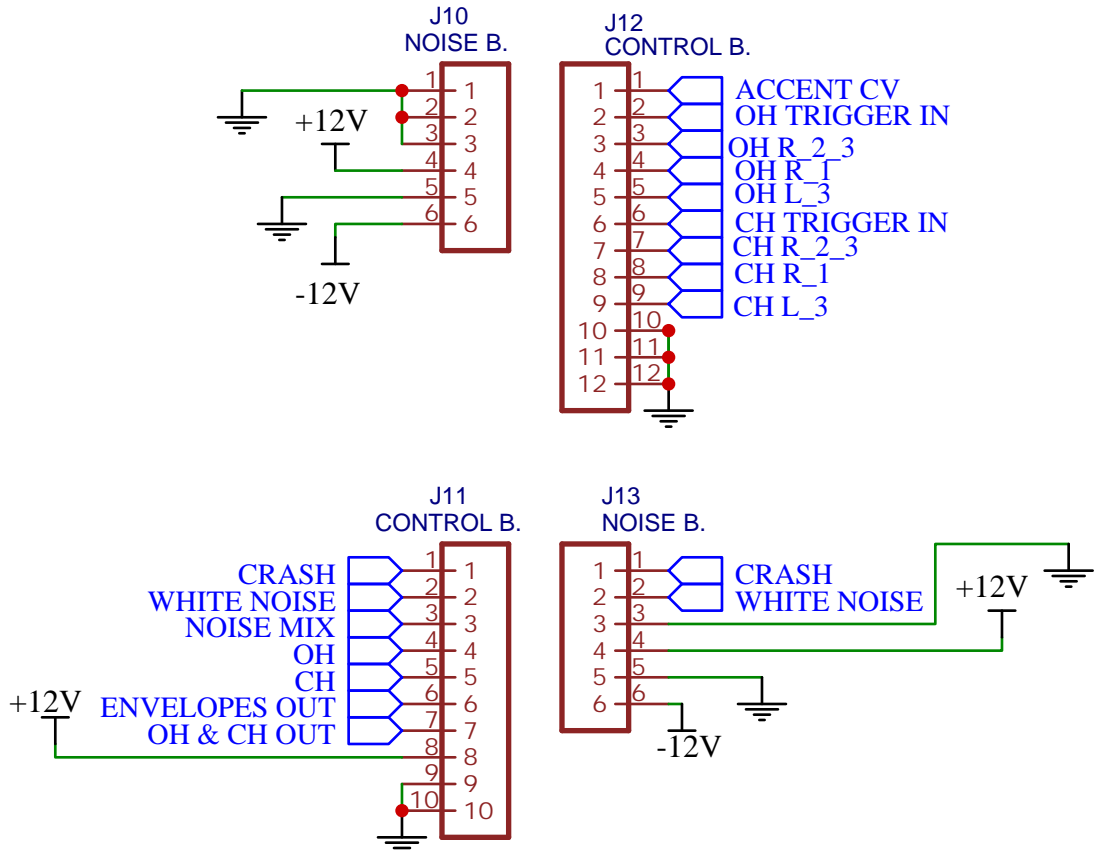


Crash (Metallic Noise)

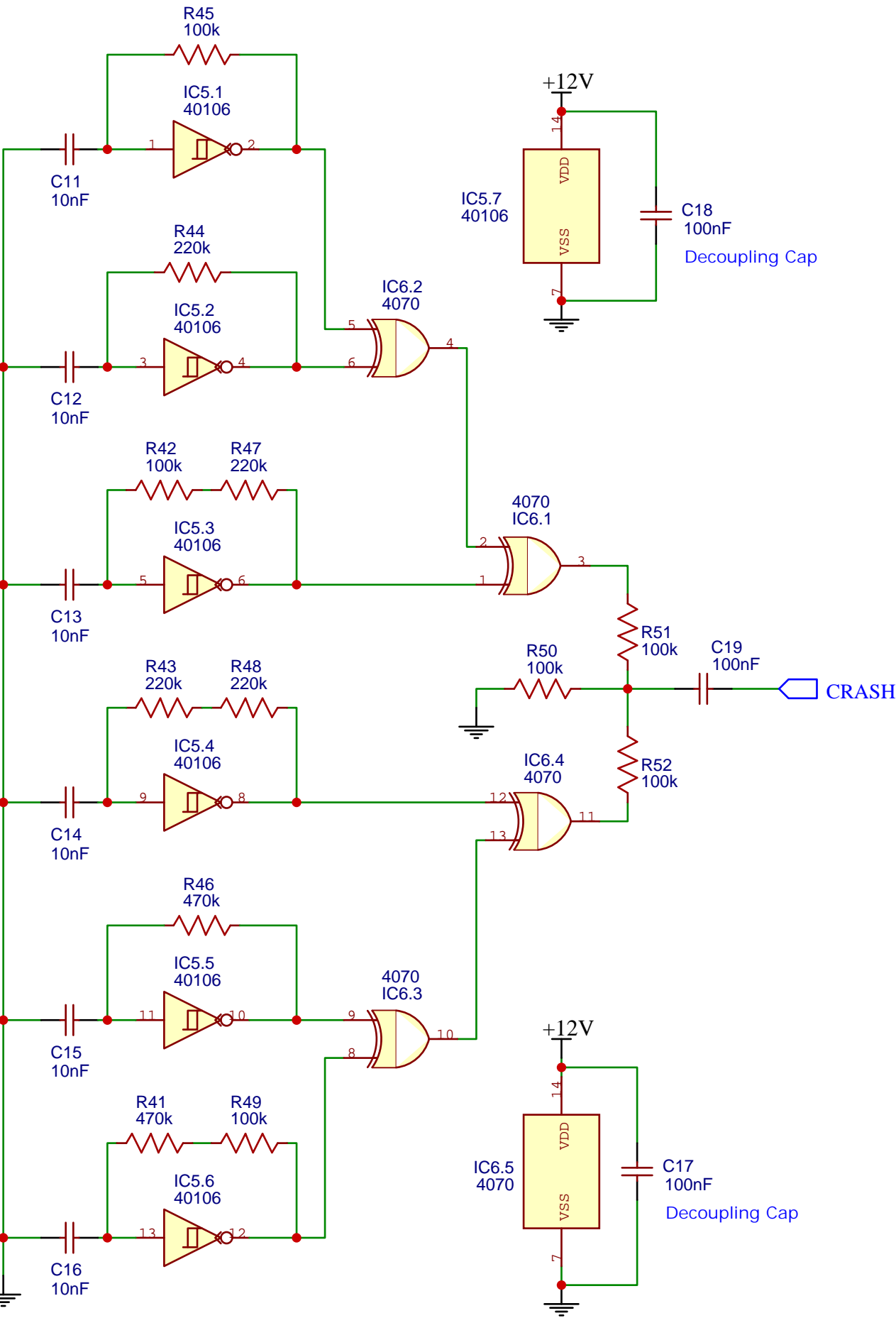Based on "LOGIC NOISE: MORE CMOS COWBELL!"
by Elliot Williams via hackaday.com




White Noise

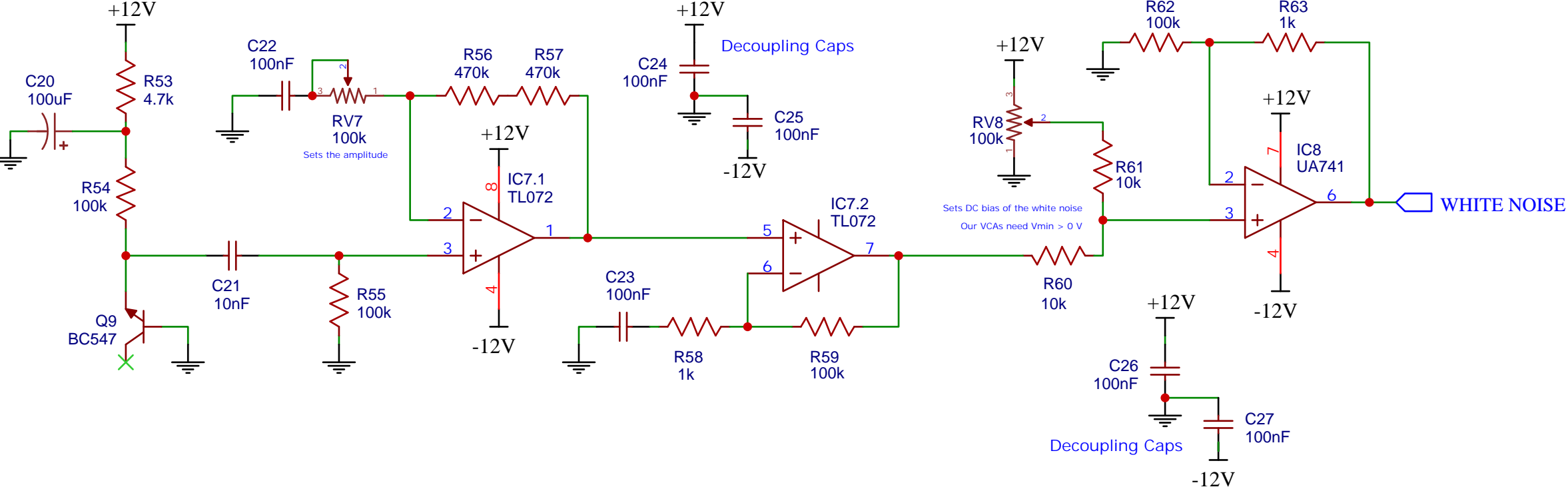Based on "White Noise Source" by Ren é Schmitz via schmitzbits.de



Board Connectors

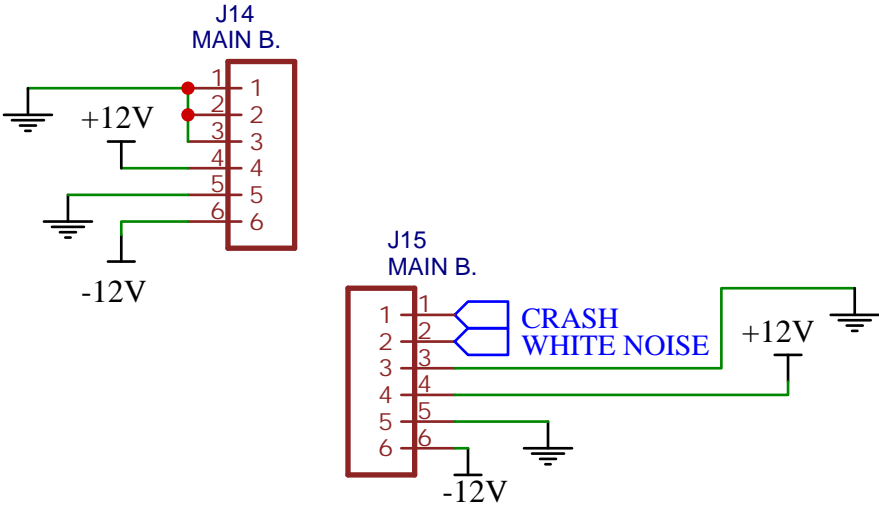

Power Supply

